

1. The formula used to determine the power requirement of an electrical device is:
  - A. watts / ohms = power
  - B. volts x ohms = power
  - C. amps x volts = power
  - D. amps x ohms = power
  
2. An emergency vehicle has a 12 volt circuit that powers two 50 watt halogen scene lights. Technician A says: A 5 amp fuse should be used to protect the circuit. Technician B says: A 15 amp fuse should be used to protect the circuit. Who is correct?
  - A. Technician A
  - B. Technician B
  - C. Both A and B
  - D. Neither A nor B
  
3. Technician A says: An inductive ammeter is connected in series. Technician B says: An inductive ammeter must be clamped onto the wire being tested. Who is correct?
  - A. Technician A
  - B. Technician B
  - C. Both A and B
  - D. Neither A nor B
  
4. Worn bushings in a cranking motor can result in which of the following?
  - A. failure of the solenoid to engage
  - B. high amp draw
  - C. high cranking speed
  - D. excessive pinion lash

## Answer Key

1. c 2. b 3. b 4. b